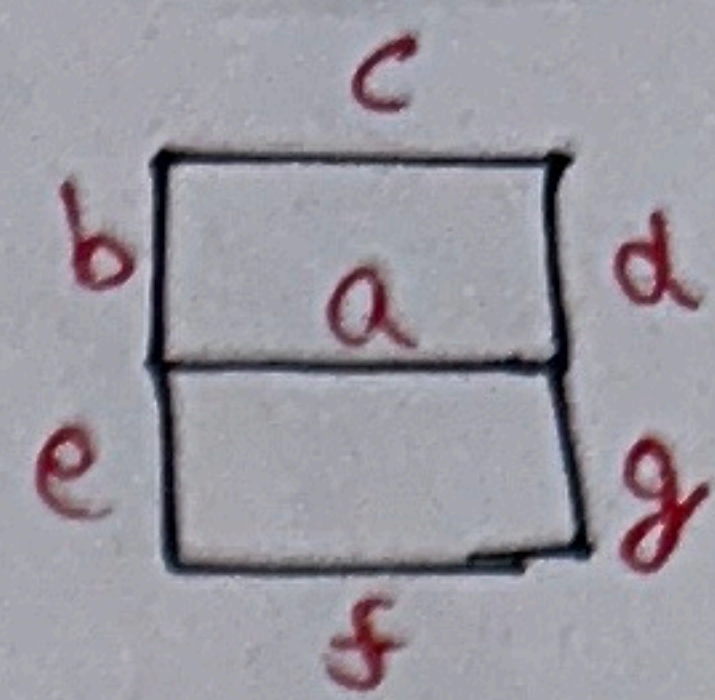


Assignment 1 : 7-segment display.

DIVYANK SHARMA

A.) Steps for logic minimisation for segment c :



	A	B	C	D	C
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	-
11	1	0	1	1	-
12	1	1	0	0	-
13	1	1	0	1	-
14	1	1	1	0	-
15	1	1	1	1	-

Don't cares.
Can be 0 or 1.


Steps for minimisation :

- 1.] To find all prime implicants. (that cannot grow further without covering 0's). = 4
- 2.] To find all distinguished 1's (1 that is covered by only one prime implicant) = 5
- 3.] Essential prime implicants (those prime implicant which covers at least one distinguished - 1). = 4

Then will see if all 1's are covered in essential implicant or any non-

essential implicant has to be added.

K-map \div

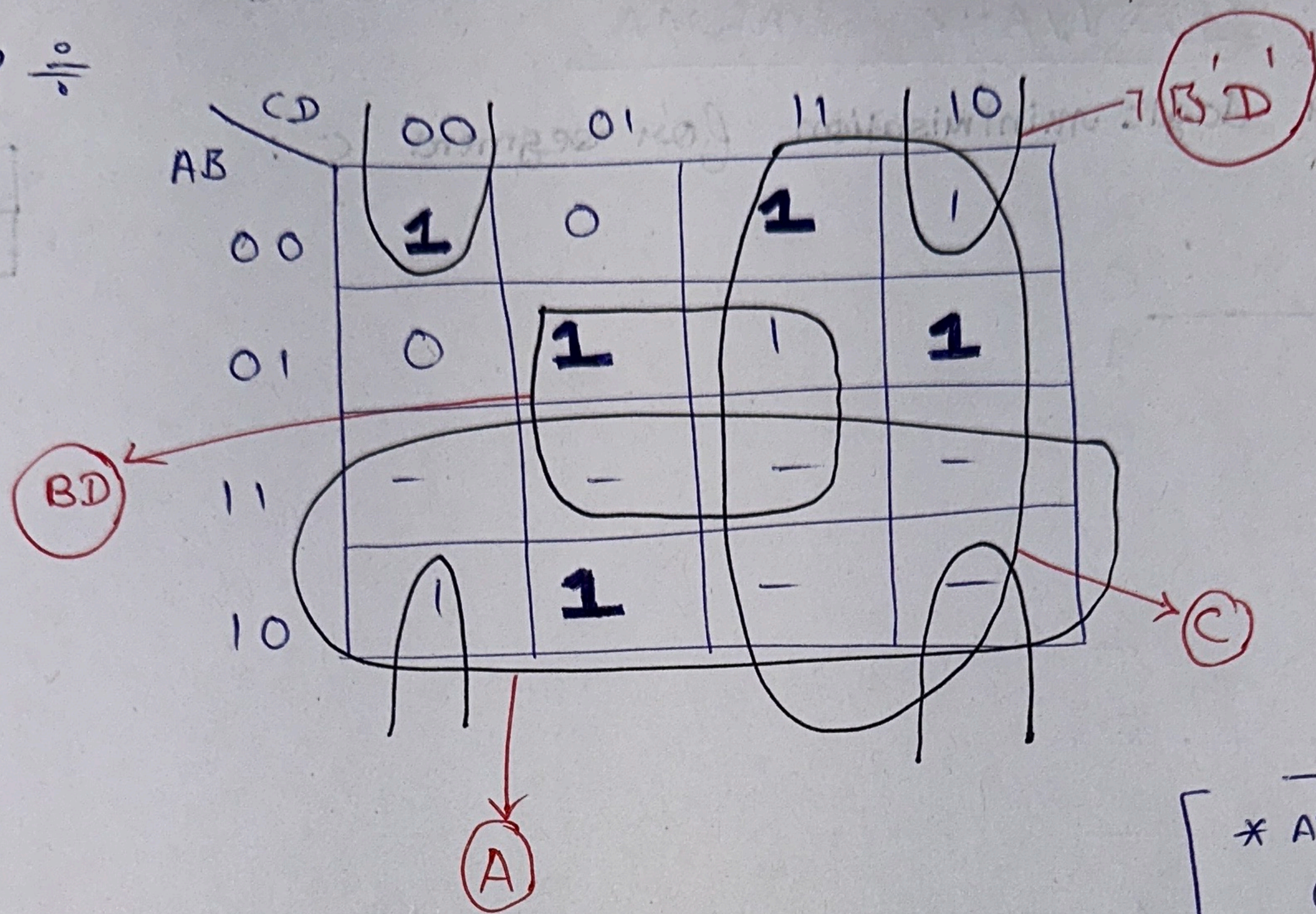

* All bold 1's are distinguished 1. and circled literals are essential literals

\div To cover all 1's we need at least 4 primes.

8 1's then one literal

4 1's then 2 literals

2 1's then 3 literals

4.) The minimal cover for segment 'c' \Rightarrow

$$f(c) = A + C + BD + B'D'$$

